

## **Term End Examination - May 2013**

Course : EEE101 - Basic Electrical and Electronic Engineering Slot: D1

Class NBR : 2179/2238/2372/2374/2377/2379/2385

Time : Three Hours Max.Marks:100

(Assumptions can be made wherever necessary)

## Answer any <u>TEN</u> Questions $(10 \times 10 = 100 \text{ Marks})$

1. For the circuit in Fig. 1, find the Thevenin equivalent between terminals a and b.

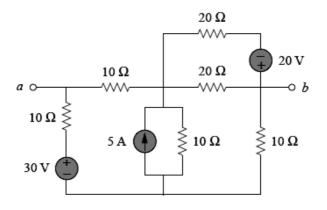


Fig. 1.

2. Obtain the node-voltage equations for the circuit in Fig. 2 by inspection. Determine the node voltages  $V_1$  and  $V_2$ .


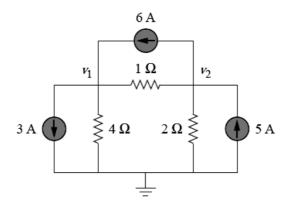


Fig. 2.

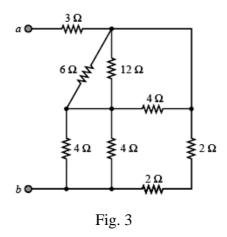3. Find the equivalent resistance between terminals a and b in the circuit of Fig. 3.



4. If  $V_0 = 8 \angle 30^{\circ}V$  in the circuit of Fig. 4, find  $I_S$ 

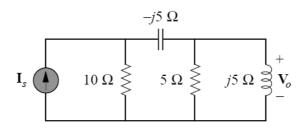


Fig. 4.

- 5. A Capacitor C is connected in series with a 40  $\Omega$  resistor across a supply of frequency 60 Hz. A current of 3A flows and the circuit impedance is 50  $\Omega$ . Calculate
  - (a) the value of the Capacitance, C,
  - (b) the supply voltage
  - (c) the phase angle between the supply voltage and current
  - (d) the potential drop across the resistor, and
  - (e) the potential drop across the capacitor

Draw the phasor diagram.

- 6. Convert the given non-standard sum-of-product Boolean expression to canonical form and simplify using K map minimization technique. Also implement the same using NOR Logic.  $F = \bar{A}C + \bar{A}B + A\bar{B}C + BC$ .
- 7. (a) Convert 8B3F<sub>16</sub> to binary.
  - (b) Convert 001101011<sub>2</sub> to octal.
  - (c) Convert  $188.54_{10}$  to binary.
  - (d) Add (-8)+(-9) using 2's complement
  - (e) Add (-8)+(9) using 2's complement

- 8. Explain Half adder and Full adder with truth table and logic diagram.
- 9. With the help of V-I Characteristics explain the working of PN Junction Diode under forward and reverse biased condition.
- 10. Explain the operating mechanism of IGBT with neat diagram.
- 11. With neat sketch brief the construction of a dc machine.
- 12. Explain the principle of operation of a synchronous motor. Also give its applications.

